 


# Lab #2

## Lab Report

---



### Introduction

The purpose of this lab is to program an FPGA to do arithmetic and use the LCD display.

---

# Results

## 1 Prelab

### Part 1.1 seg7.v Draft

```
//Verilog seg7.v module.
```

```
module seg7(bcd, seg);
```

```
    //Declare inputs, outputs, and internal variables.
```

```
    input [3:0] bcd;
```

```
    output [6:0] seg;
```

```
    reg [6:0] seg;
```

```
    //always block
```

```
    always @(bcd)
```

```
    Begin
```

```
        //case statement
```

```
        case (bcd)
```

```
            0 : seg = 7'b0000001;
```

```
            1 : seg = 7'b1001111;
```

```
            2 : seg = 7'b0010010;
```

```
            3 : seg = 7'b0000110;
```

```
            4 : seg = 7'b1001100;
```

```
            5 : seg = 7'b0100100;
```

```
            6 : seg = 7'b0100000;
```

```
            7 : seg = 7'b0001111;
```

```
            8 : seg = 7'b0000000;
```

```
            9 : seg = 7'b0000100;
```

```
        //if not a bcd number, switch off 7 segment display.
```

---

```
        default : seg = 7'b11111111;
    endcase
end

endmodule
```

**Figure 1.1.1** seg7.v Draft Code.

## **Part 1.2** fa.v Draft

```
//Verilog fa.v module.
module fa (in1, in2, cin, sum, cout);

    //Declare inputs, outputs, and internal variables.
    input in1,
           in2,
           cin;
    output sum,
           Cout;

    // use Boolean expressions
    assign Sum  = (in1 ^ in2) ^ cin;
    assign Cout = (in1 & in2) | (in2 & cin) | (cin & in1);
endmodule
```

**Figure 1.2.1** fa.v Draft Code.

---

### 1.3 add4bit.v Draft

//Verilog add4bit.v module.

```
module add4bit(a,b,cin,sum,cout);

    //Declare inputs, outputs, and internal variables.
    input [3:0]a,b;
    input cin;
    output wire [3:0]sum;
    output cout;

    // instantiating four full-adder circuits - ripple carry
    fa FA1(a[0],b[0],cin,sum[0],cout1);
    fa FA2(a[1],b[1],cout1,sum[1],cout2);
    fa FA3(a[2],b[2],cout2,sum[2],cout3);
    fa FA4(a[3],b[3],cout3,sum[3],cout);
endmodule
```

---

## **Discussion**

When we ...

## **Conclusion**

We can see ...